



Introduction to Digital Design

Week 15: Programmable Processors and HDL

Yao Zheng
Assistant Professor
University of Hawai'i at Mānoa
Department of Electrical Engineering

Overview


- Programmable processors are widely used
 - Easy availability, short design time
- Basic architecture
 - Datapath with register file and ALU
 - Control unit with PC, IR, and controller
 - Memories for instructions and data
 - Control unit fetches, decodes, and executes
- Three-instruction processor with machine-level programs
 - Extended to six instructions
 - Real processors have dozens or hundreds of instructions
 - Extended to access external pins
 - Modern processors are far more sophisticated
- Hardware Description Languages (HDLs)
 - VHDL, Verilog, and SystemC are popular
 - Introduced languages mainly through examples

2


Programmable Processor

 8.1


- Programmable (general-purpose) processor
 - Mass-produced, then programmed to implement different processing tasks
 - Well-known common programmable processors: Pentium, Sparc, PowerPC
 - Lesser-known but still common: ARM, MIPS, 8051, PIC, AVR
 - Low-cost embedded processors found in cell phones, blinking shoes, etc.
 - Instructive to design a very simple programmable processor
 - Real processors can be much more complex



 Seatbelt warning light single-purpose processor



 3-tap FIR filter single-purpose processor



General-purpose processor


Note: Slides with animations are denoted with a small red "a" near the animated items

3

Basic Architecture

 8.2

- Processing generally consists of:
 - Loading some data
 - Transforming that data
 - Storing that data
- **Basic datapath:** Useful circuit in a programmable processor
 - Can read/write data memory, where main data exists
 - Has register file to hold data locally
 - Has ALU to transform local data



Datapath

4

Basic Datapath Operations

- Load operation: Load data from data memory to RF
- ALU operation: Transforms data by passing one or two RF register values through ALU, performing operation (ADD, SUB, AND, OR, etc.), and writing back into RF.
- Store operation: Stores RF register value back into data memory
- Each operation can be done in one clock cycle



Load operation



ALU operation



Store operation


5

Basic Datapath Operations


- **Q:** Which are valid *single-cycle operations* for given datapath?
 - Move D[1] to RF[1] (i.e., $RF[1] = D[1]$)
 - A: YES – That's a load operation
 - Store RF[1] to D[9] and store RF[2] to D[10]
 - A: NO – Requires two separate store operations
 - Add D[0] plus D[1], store result in D[9]
 - A: NO – ALU operation (ADD) only works with RF. Requires two load operations (e.g., $RF[0]=D[0]$; $RF[1]=D[1]$), an ALU operation (e.g., $RF[2]=RF[0]+RF[1]$), and a store operation (e.g., $D[9]=RF[2]$)



Load operation

 

ALU operation

 

Store operation


6

Basic Architecture – Control Unit

- $D[9] = D[0] + D[1]$ – requires a sequence of four datapath operations:

```
0: RF[0] = D[0]
1: RF[1] = D[1]
2: RF[2] = RF[0] + RF[1]
3: D[9] = RF[2]
```


- Each operation is an *instruction*
 - Sequence of instructions – *program*
 - Looks cumbersome, but that's the world of programmable processors – Decomposing desired computations into processor-supported operations
 - Store program in *Instruction memory*
 - *Control unit* reads each instruction and executes it on the datapath
 - PC: Program counter – address of current instruction
 - IR: Instruction register – current instruction

 

7

Basic Architecture – Control Unit

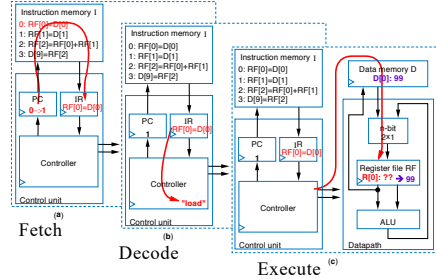
- To carry out *each instruction*, the control unit must:
 - **Fetch** – Read instruction from inst. mem.
 - **Decode** – Determine the operation and operands of the instruction
 - **Execute** – Carry out the instruction's operation using the datapath



8

Basic Architecture – Control Unit

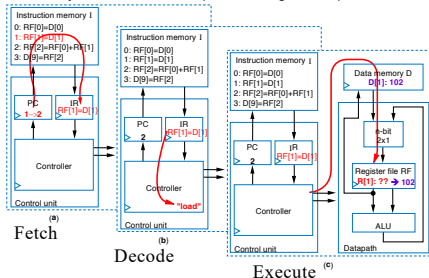
- To carry out *each instruction*, the control unit must:
 - **Fetch** – Read instruction from inst. mem.
 - **Decode** – Determine the operation and operands of the instruction
 - **Execute** – Carry out the instruction's operation using the datapath



9

Basic Architecture – Control Unit

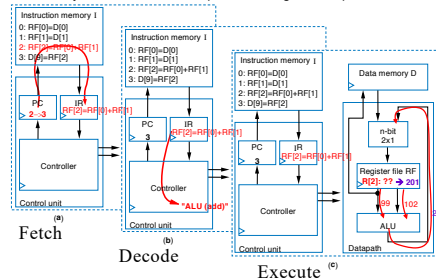
- To carry out *each instruction*, the control unit must:
 - **Fetch** – Read instruction from inst. mem.
 - **Decode** – Determine the operation and operands of the instruction
 - **Execute** – Carry out the instruction's operation using the datapath



10

Basic Architecture – Control Unit

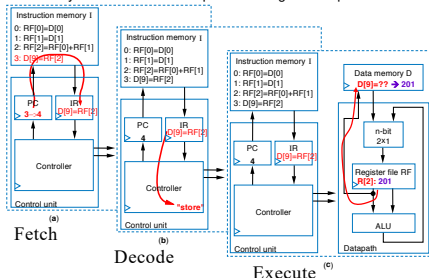- To carry out *each instruction*, the control unit must:
 - **Fetch** – Read instruction from inst. mem.
 - **Decode** – Determine the operation and operands of the instruction
 - **Execute** – Carry out the instruction's operation using the datapath



11

Basic Architecture – Control Unit


To summarize, the control unit processes each instruction in three stages:

1. first *fetching* the instruction by loading the current instruction into *IR* and incrementing the *PC* for the next fetch,
2. next *decoding* the instruction to determine its operation, and
3. finally *executing* the operation by setting the appropriate control lines for the datapath, if applicable. If the operation is a datapath operation, the operation may be one of three possible types:

(a) *loading* a data memory location into a register file location,

(b) transforming data using an *ALU* operation on register file locations and writing results back to a register file location, or

 (c) *storing* a register file location into a data memory location.



12

Creating a Sequence of Instructions

- **Q:** Create sequence of instructions to compute $D[3] = D[0] + D[1] + D[2]$ on earlier-introduced processor
- **A1:** One possible sequence
 - First load data memory locations into register file
 - $R[3] = D[0]$
 - $R[4] = D[1]$
 - $R[2] = D[2]$
 (Note arbitrary register locations)
 - Next, perform the additions
 - $R[1] = R[3] + R[4]$
 - $R[1] = R[1] + R[2]$
 - Finally, store result
 - $D[3] = R[1]$
- **A2:** Alternative sequence
 - First load $D[0]$ and $D[1]$ and add them
 - $R[1] = D[0]$
 - $R[2] = D[1]$
 - $R[1] = R[1] + R[2]$
 - Next, load $D[2]$ and add
 - $R[2] = D[2]$
 - $R[1] = R[1] + R[2]$
 - Finally, store result
 - $D[3] = R[1]$

13


Number of Cycles

- **Q:** How many cycles are needed to execute six instructions using the earlier-described processor?
- **A:** Each instruction requires 3 cycles – 1 to fetch, 1 to decode, and 1 to execute
 - Thus, $6 \text{ instr} * 3 \text{ cycles/instr} = 18 \text{ cycles}$

14


Three-Instruction Programmable Processor

 - Instruction Set – List of allowable instructions and their representation in memory, e.g.,
 - **Load** instruction – 0000 $r_3 r_2 r_1 r_0 d_7 d_6 d_5 d_4 d_3 d_2 d_1 d_0$
 - **Store** instruction – 0001 $r_3 r_2 r_1 r_0 d_7 d_6 d_5 d_4 d_3 d_2 d_1 d_0$
 - **Add** instruction – 0010 $r_a r_3 r_a r_2 r_a r_1 r_a r_0 r_b r_b r_b r_b r_c r_c r_c r_c$



15

Program for Three-Instruction Processor

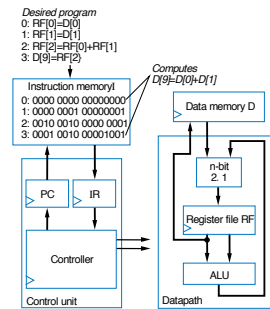

16

Program for Three-Instruction Processor

- Another example program in machine code
 - Compute $D[5] = D[5] + D[6] + D[7]$

```

0: 0000 0000 00000101 // RF[0] = D[5]
1: 0000 0001 00000110 // RF[1] = D[6]
2: 0000 0010 00000111 // RF[2] = D[7]
3: 0010 0000 0000 0001 // RF[0] = RF[0] + RF[1]
                        // which is D[5]+D[6]
4: 0010 0000 0000 0010 // RF[0] = RF[0] + RF[2]
                        // now D[5]+D[6]+D[7]
5: 0001 0000 00000101 // D[5] = RF[0]

```

– **Load** instruction – 0000 $r_3 r_2 r_1 r_0 d_7 d_6 d_5 d_4 d_3 d_2 d_1 d_0$
 – **Store** instruction – 0001 $r_3 r_2 r_1 r_0 d_7 d_6 d_5 d_4 d_3 d_2 d_1 d_0$
 – **Add** instruction – 0010 $r_a r_3 r_a r_2 r_a r_1 r_a r_0 r_b r_b r_b r_b r_c r_c r_c r_c$

17

Assembly Code

- Machine code (0s and 1s) hard to work with
- **Assembly code** – Uses mnemonics
 - **Load** instruction – **MOV Ra, d**
 - specifies the operation $RF[a]=D[d]$, a must be 0, 1, ..., or 15—so $R0$ means $RF[0]$, $R1$ means $RF[1]$, etc. d must be 0, 1, ..., 255
 - **Store** instruction – **MOV d, Ra**
 - specifies the operation $D[d]=RF[a]$
 - **Add** instruction – **ADD Ra, Rb, Rc**
 - specifies the operation $RF[a]=RF[b]+RF[c]$

Desired program

```

0: RF[0]=D[0]
1: RF[1]=D[1]
2: RF[2]=RF[0]+RF[1]
3: D[9]=RF[2]

```

```

0: 0000 0000 00000000
1: 0000 0001 00000001
2: 0010 0010 0000 0001
3: 0001 0010 0000 1001

```

machine code

```

0: MOV R0, 0
1: MOV R1, 1
2: ADD R2, R0, R1
3: MOV 9, R2


```

assembly code

18

Control-Unit and Datapath for Three-Instruction Processor

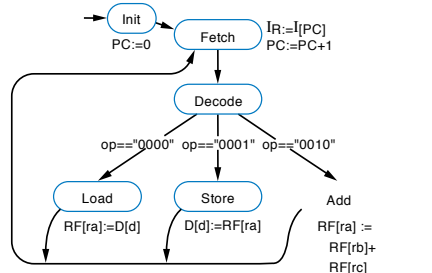
- To design the processor, we can begin with a high-level state machine description of the processor's behavior



19

Control-Unit and Datapath for Three-Instruction Processor

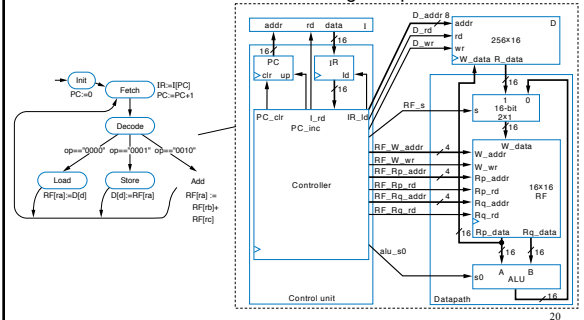
- Create detailed connections among components



20

Control-Unit and Datapath for Three-Instruction Processor

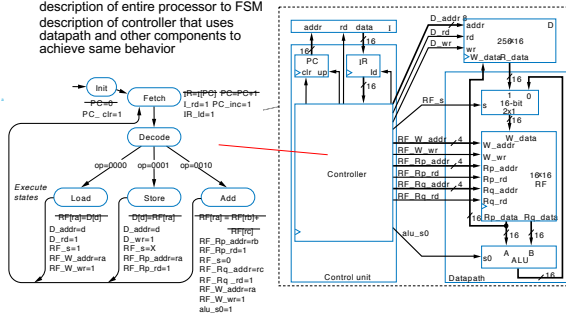- Convert high-level state machine description of entire processor to FSM description of controller that uses datapath and other components to achieve same behavior



21

A Six-Instruction Programmable Processor

8.4

- Let's add three more instructions:
 - Load-constant** instruction—**0011** $r_3 r_2 r_1 r_0$ $c_7 c_6 c_5 c_4 c_3 c_2 c_1 c_0$
 - MOV Ra, #c**—specifies the operation $RF[a] = c$
 - Subtract** instruction—**0100** $r_3 r_2 r_1 r_0$ $r_b r_b r_b r_b r_b r_b r_b r_b$ $r_c r_c r_c r_c r_c r_c r_c r_c$
 - SUB Ra, Rb, Rc**—specifies the operation $RF[a] = RF[b] - RF[c]$
 - Jump-if-zero** instruction—**0101** $r_3 r_2 r_1 r_0$ $o_7 o_6 o_5 o_4 o_3 o_2 o_1 o_0$
 - JMPZ Ra, offset**—specifies the operation $PC = PC + offset$ if $RF[a] = 0$

TABLE 8.1 Six-instruction instruction set.

Instruction	Meaning
MOV Ra, d	$RF[a] = D[d]$
MOV d, Ra	$D[d] = RF[a]$
ADD Ra, Rb, Rc	$RF[a] = RF[b] + RF[c]$
MOV Ra, #C	$RF[a] = C$
SUB Ra, Rb, Rc	$RF[a] = RF[b] - RF[c]$
JMPZ Ra, offset	$PC = PC + offset$ if $RF[a] = 0$


TABLE 8.2 Instruction opcodes.

Instruction	Opcodes
MOV Ra, d	0000
MOV d, Ra	0001
ADD Ra, Rb, Rc	0010
MOV Ra, #C	0011
SUB Ra, Rb, Rc	0100
JMPZ Ra, offset	0101

22

Extending the Control-Unit and Datapath

- The **load constant** instruction requires that the register file be able to load data from $IR[7..0]$, in addition to data from data memory or the ALU output. Thus, we widen the register file's multiplexer from 2x1 to 3x1, add another mux control signal, and also create a new signal coming from the controller labeled RF_W_data , which will connect with $IR[7..0]$.
- The **subtract** instruction requires that we use an ALU capable of subtraction, so we add another ALU control signal.
- The **jump-if-zero** instruction requires that we be able to detect if a register is zero, and that we be able to add $IR[7..0]$ to the PC.
 - We insert a datapath component to detect if the register file's R_p read port is all zeros (that component would just be a NOR gate).
 - We also upgrade the PC register so it can be loaded with PC plus $IR[7..0]$. The adder used for this also subtracts 1 from the sum, to compensate for the fact that the **Fetch** state already added 1 to the PC .

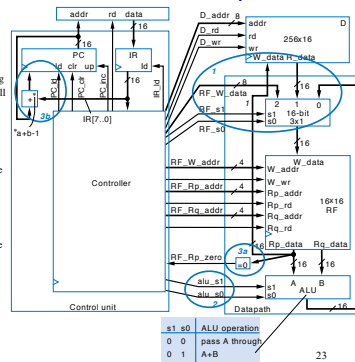

23

Controller FSM for the Six-Instruction Processor

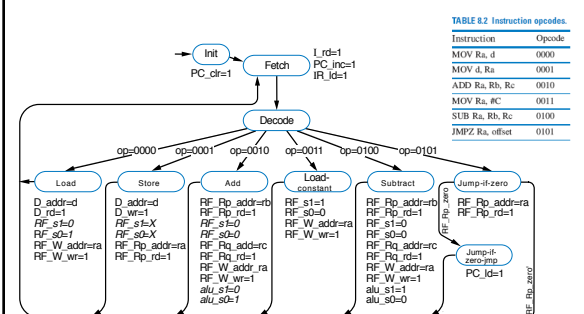


TABLE 8.2 Instruction opcodes.

Instruction	Opcodes
MOV Ra, d	0000
MOV d, Ra	0001
ADD Ra, Rb, Rc	0010
MOV Ra, #C	0011
SUB Ra, Rb, Rc	0100
JMPZ Ra, offset	0101

24

Program for the Six-Instruction Processor

- Example program – Count number of non-zero words in D[4] and D[5]
 - Result will be either 0, 1, or 2
 - Put result in D[9]

```

MOV R0, #0; // initialize result to 0      0011 0000 00000000
MOV R1, #1; // constant 1 for incrementing 0011 0001 00000001
MOV R2, 4; // get data memory location 4  0000 0010 00000100
JMPZ R2, lab1; // if zero, skip next instruction 0101 0010 00000010
ADD R0, R0, R1; // not zero, so increment result 0010 0000 0000 0001
lab1: MOV R2, 5; // get data memory location 5 0000 0010 00000101
JMPZ R2, lab2; // if zero, skip next instruction 0101 0010 00000010
ADD R0, R0, R1; // not zero, so increment result 0010 0000 0000 0001
lab2: MOV R0, 9; // store result in data memory location 9 0001 0000 00001001

```

(a)

TABLE 8.2 Instruction opcodes.

Instruction	Opcode
MOV R _a , d	0000
MOV d, R _a	0001
ADD R _a , R _b , R _c	0010
MOV R _a , #c	0011
SLB R _a , R _b , R _c	0100
JMPZ R _a , offset	0101

(b)

25

Further Extensions to the Programmable Processor


8.5

- Typical processor instruction set will contain dozens of data movement (e.g., loads, stores), ALU (e.g., add, sub), and flow-of-control (e.g., jump) instructions


- Extending the control-unit/datapath follows similarly to previously-shown extensions

- Input/output extensions

 - Certain memory locations may actually be external pins
 - e.g., D[240] may represent 8-bit input I0, D[255] may represent 8-bit output P7



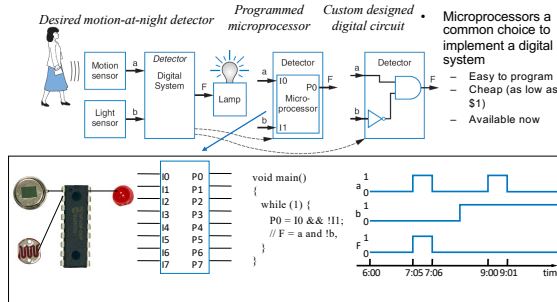Program using I/O Extensions – Recall Chpt 1 C-Program Example



27


Program Using Input/Output Extensions

Underlying assembly code for C expression I0 && !I1.

```

0: MOV R0, 240 // move D[240], which is the value at pin I0, into R0
1: MOV R1, 241 // move D[241], which is that value at pin I1, into R1
2: NOT R1, R1 // compute !I1, assuming existence of a complement instruction
3: AND R0, R0, R1 // compute I0 && !I1, assuming an AND instruction
4: MOV 248, R0 // move result to D[248], which is pin P0

```

 


28

Hardware description language

 9.1

- A drawing of a circuit, or *schematic*, contains graphical information about a design
 - Inverter is above the OR gate, AND gate is to the right, etc.
- Such graphical information may not be useful for large designs
- Can use textual language instead




29

Note: Slides with animation are denoted with a small red "A" near the animated items.

Textual Language – English

 - Can describe circuit using English text rather than using a drawing
 - Of course, English isn't a good language for a computer to read
 - Need a more precise, computer-oriented language



(b) We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:

- An inverter, which has a bit input x, and bit output F.
- A 2-input OR gate, which has inputs x and y, and bit output F.
- A 2-input AND gate, which has bit inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.

The DoorOpener circuit internally consists of:

- An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.
- A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
- A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.

That's all.

30

Computer-Readable Textual Language for Describing Hardware Circuits: HDLs

- Hardware description language (HDL)
 - Intended to describe circuits textually, for a computer to read
 - Evolved starting in the 1970s and 1980s
- Popular languages today include:
 - VHDL –Defined in 1980s by U.S. military; Ada-like language
 - Verilog –Defined in 1980s by a company; C-like language
 - SystemC –Defined in 2000s by several companies; consists of libraries in C++


31

Combinational Logic Description using Hardware Description Languages

 9.2

• Structure

- Another word for "circuit"
- An interconnection of components
- Key use of HDLs is to describe structure



Note: The term "instantiate" will be used to indicate adding a new copy of a component to a circuit

The OR component




Three instances of the OR component



32

Describing Structure in VHDL

 - Entity – Defines new item's name & ports (inputs/outputs)
 - std_logic means bit type, defined in ieee library
- Architecture – Describes internals, which we named "circuit"
 - Declares 3 previously-defined components
 - Declares internal signals
 - Note "--" comment
 - Instantiates and connects those components



We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:
An inverter, which has a bit input x, and bit output F.
A 2-input OR gate, which has inputs x and y, and bit output F.
A 2-input AND gate, which has inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.
The DoorOpener circuit internally consists of:
An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.
A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.
That's all.


```
library ieee;
use ieee.std_logic_1164.all;
entity DoorOpener is
    port (
        c, h, p: in std_logic;
        f: out std_logic
    );
end DoorOpener;

architecture Circuit of DoorOpener is
    component Inv
        port (
            x: in std_logic;
            F: out std_logic
        );
    end component;
    component OR2
        port (
            x, y: in std_logic;
            F: out std_logic
        );
    end component;
    component AND2
        port (
            x, y: in std_logic;
            F: out std_logic
        );
    end component;
    signal n1, n2: std_logic; --internal wires
begin
    Inv_1: Inv port map (x=c, F=n1);
    OR2_1: OR2 port map (x=h, y=p, F=n2);
    AND2_1: AND2 port map (x=n1, y=n2, F=f);
end Circuit;
```

33

Describing Structure in Verilog

 - Modules defined for Inv, OR2, and AND2 (details omitted)
 - Note "//" comment
- Module defined for DoorOpener
 - Lists inputs and outputs
 - Declares internal wires
 - Instantiates and connects three components



We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:
An inverter, which has a bit input x, and bit output F.
A 2-input OR gate, which has inputs x and y, and bit output F.
A 2-input AND gate, which has inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.
The DoorOpener circuit internally consists of:
An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.
A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.
That's all.

```
module Inv(x, F);
    input x;
    output F;
    // details not shown
endmodule

module OR2(x, y, F);
    input x, y;
    output F;
    // details not shown
endmodule


module AND2(x, y, F);
    input x, y;
    output F;
    // details not shown
endmodule

module DoorOpener(c, h, p, f);
    input c, h, p;
    output f;
    wire n1, n2;
    Inv Inv_1(c, n1);
    OR2 OR2_1(h, p, n2);
    AND2 AND2_1(n1, n2, f);
endmodule
```

34

Describing Structure in SystemC

 - Module defined
 - Declares inputs and outputs
 - Declares internal wires
 - Note "//" comment
 - Declares three previously-defined components
 - Constructor function "CTOR"
 - Instantiates components
 - Connects components



We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:
An inverter, which has a bit input x, and bit output F.
A 2-input OR gate, which has inputs x and y, and bit output F.
A 2-input AND gate, which has inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.
The DoorOpener circuit internally consists of:
An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.
A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.
That's all.

```
#include "systemc.h"
#include "inv.h"
#include "or2.h"
#include "and2.h"

SC_MODULE(DoorOpener)
{
    sc_in<sc_logic> c, h, p;
    sc_out<sc_logic> f;
    // internal wires
    sc_signal<sc_logic> n1, n2;
    // component declarations
    Inv Inv_1;
    OR2 OR2_1;
    AND2 AND2_1;
    // component instantiations
    SC_CTOR(DoorOpener): Inv_1("Inv_1"),
        OR2_1("OR2_1"), AND2_1("AND2_1")
    {
        Inv_1->x(c);
        Inv_1->F(n1);
        OR2_1->x(h);
        OR2_1->y(p);
        OR2_1->F(n2);
        AND2_1->x(n1);
        AND2_1->y(n2);
        AND2_1->F(f);
    }
};
```

35

Combinational Behavior

• Combinational behavior

- Description of desired behavior of combinational circuit without creating circuit itself
- e.g., $F = c' * (h + p)$ can be described as equation rather than circuit
- HDLs support description of combinational behavior

36

Describing Combinational Behavior in VHDL

- Describing an OR gate's behavior
 - Entity defines input/output ports
 - Architecture
 - Process – Describes behavior
 - Process "sensitive" to x and y
 - Means behavior only executes when x changes or y changes
 - Behavior assigns a new value to output port F, computed using built-in operator "or"

```
library ieee;
use ieee.std_logic_1164.all;

entity OR2 is
  port (x, y: in std_logic;
        F: out std_logic);
end OR2;

architecture behavior of OR2 is
  process (x, y)
  begin
    F <= x or y;
  end process;
end behavior;
```

37

Describing Combinational Behavior in VHDL

- Describing a custom function's behavior
 - Desired function: $f = c''(h+p)$
 - Entity defines input/output ports (not shown)
 - Architecture
 - Process
 - Sensitive to c, h, and p
 - Assigns a new value to output port f, computed using built-in operators "not", "and", and "or"

```
architecture beh of DoorOpener is
begin
  process(c, h, p)
  begin
    f <= not(c) and (h or p);
  end process;
end beh;
```

38

Describing Combinational Behavior in Verilog

- Describing an OR gate's behavior
 - Module declares input/output ports
 - Also indicates that F is "reg"
 - Means F stores value
 - By default, ports are wires, having no storage
 - "always" procedure executes statement block when change occurs on x or on y
 - "Sensitive" to x and y
 - Assigns value to F, computed using built-in OR operator "|"

```
module OR2(x,y,F);
  input x, y;
  output F;
  reg F;

  always @(x or y)
  begin
    F <= x | y;
  end
endmodule
```

39

Describing Combinational Behavior in Verilog

- Describing a custom function's behavior
 - Desired function: $f = c''(h+p)$
 - Module defines input/output ports
 - Output f defined as "reg"
 - "always" procedure sensitive to inputs
 - Assigns value to f, computed using built-in operators for NOT (~), AND (&), and OR (|)

```
module DoorOpener(c,h,p,f);
  input c, h, p;
  output f;
  reg f;

  always @(c or h or p)
  begin
    f <= (~c) & (h | p);
  end
endmodule
```

40

Describing Combinational Behavior in SystemC

- Describing an OR gate's behavior
 - Module declares input/output ports
 - Constructor (CTOR)
 - Indicates module described by a method (procedure) "comblgic"
 - Sensitive to x and y
 - Method "comblgic" assigns F a new value using built-in OR operator "|"
 - Reading input port done using .read() function defined for input port type; likewise, writing done using .write() function

```
#include "systemc.h"

SC_MODULE(OR2)
{
  sc_in<sc_logic> x, y;
  sc_out<sc_logic> F;

  SC_CTOR(OR2)
  {
    SC_METHOD(comblgic);
    sensitive << x << y;
  }

  void comblgic()
  {
    F.write(x.read() | y.read());
  }
};
```

41

Describing Combinational Behavior in SystemC

- Describing a custom function's behavior
 - Desired function: $f = c''(h+p)$
 - Module defines input/output ports
 - Constructor
 - Indicates module described by a method (procedure) "comblgic"
 - Sensitive to c, h, and p
 - "comblgic" method
 - Assigns value to f, computed using built-in operators for NOT (~), AND (&), and OR (|)

```
#include "systemc.h"

SC_MODULE(DoorOpener)
{
  sc_in<sc_logic> c, h, p;
  sc_out<sc_logic> f;

  SC_CTOR(DoorOpener)
  {
    SC_METHOD(comblgic);
    sensitive << c << h << p;
  }


  void comblgic()
  {
    f.write((~c.read()) & (h.read() | p.read()));
  }
};
```

42

Testbenches

• Testbench

 - Assigns values to a system's inputs, check that system outputs correct values
- A key use of HDLs is to simulate system to ensure design is correct



43

Testbench in VHDL

- Entity
 - No inputs or outputs
- Architecture
 - Declares component to test, declares signals
 - Instantiates component, connects to signals
 - Process writes input signals, checks output signal
 - Waits a small amount of time after writing input signals
 - Checks for correct output value using "assert" statement

```
library ieee;
use ieee.std_logic_1164.all;


entity Testbench is
end Testbench;

architecture behavior of Testbench is
  component DoorOpener
    port ( c, h, p: in std_logic;
          f: out std_logic
        );
  end component;
  signal c, h, p, f: std_logic;
begin
  DoorOpener1: DoorOpener port map (c,h,p,f);

  process
  begin
    -- case 0
    c <= '0'; h <= '0'; p <= '0';
    wait for 1 ns;
    assert (f='0') report "Case 0 failed";

    -- case 1
    c <= '0'; h <= '0'; p <= '1';
    wait for 1 ns;
    assert (f='1') report "Case 1 failed";
    -- (cases 2-6 omitted from figure)

     -- case 7
    c <= '1'; h <= '1'; p <= '1';
    wait for 1 ns;
    assert (f='0') report "Case 7 failed";
    wait; -- process does not wake up again
  end process;
end behavior;
```



44

Testbench in Verilog


• Module

- Three register signals for inputs (values must be written and stored)
- One wire signal for output (value is only read, need not be stored)
- Instantiates component, connects to signals
- "initial" procedure executed only once at beginning
 - Sets input values
 - Displays output value

```
module Testbench;
  reg c, h, p;
  wire f;

  DoorOpener DoorOpener1(c, h, p, f);

   initial
  begin
    // case 0
    c <= 0; h <= 0; p <= 0;
    #1 $display("f = %b", f);
    // case 1
    c <= 0; h <= 0; p <= 1;
    #1 $display("f = %b", f);
    // (cases 2-6 omitted from figure)
    // case 7
    c <= 1; h <= 1; p <= 1;
    #1 $display("f = %b", f);
  end
endmodule
```



45

Testbench in SystemC

• Module

- Testbench is its own module
- Three outputs, one for each input of system to test
- One input, for the one output of the system to test
- Constructor defined as THREAD
 - Like MODULE, but allows use of "wait" to control timing
- testbench procedure writes outputs, waits for small amount of time, checks for correct output
 - assert function prints error if condition is not true


```
#include "systemc.h"

SC_MODULE(Testbench)
{
  sc_out<sc_logic> c_t, h_t, p_t;
  sc_in<sc_logic> f_t;

  SC_CTOR(Testbench)
  {
    SC_THREAD(testbench_proc);
  }

  void testbench_proc()
  {
    // case 0
    c_t.write(SC_LOGIC_0);
    h_t.write(SC_LOGIC_0);
    p_t.write(SC_LOGIC_0);
    wait(1, SC_NS);
    assert( f_t.read() == SC_LOGIC_0 );

     // case 1
    c_t.write(SC_LOGIC_0);
    h_t.write(SC_LOGIC_0);
    p_t.write(SC_LOGIC_1);
    wait(1, SC_NS);
    assert( f_t.read() == SC_LOGIC_1 );
    // (cases 2-6 omitted from figure)
    // case 7
    c_t.write(SC_LOGIC_1);
    h_t.write(SC_LOGIC_1);
    p_t.write(SC_LOGIC_1);
    wait(1, SC_NS);
    assert( f_t.read() == SC_LOGIC_0 );
  }
  SC_STOP();
}
```



46

Sequential Logic Description using Hardware Description Languages

9.3

- Will consider description of three sequential components
 - Registers
 - Oscillators
 - Controllers

47

Describing a 4-bit Register in VHDL

- Entity
 - 4 data inputs, 4 data outputs, and a clock input
 - Use std_logic_vector for 4-bit data
 - l: in std_logic_vector(3 downto 0)
 - l <= "1000" would assign l(3)=1, l(2)=0, l(1)=0, l(0)=0
- Architecture
 - Process sensitive to clock input
 - First statement detects if change on clock was a rising edge
 - If clock change was rising edge, sets output Q to input l
 - Ports are signals, and signals store values – thus, output retains new value until set to another value

```
library ieee;
use ieee.std_logic_1164.all;

entity Reg4 is
  port ( l: in std_logic_vector(3 downto 0);
        Q: out std_logic_vector(3 downto 0);
        clk: in std_logic
      );
end Reg4;

architecture behavior of Reg4 is
  begin
    process(clk)
    begin
      if (clk='1' and clk'event) then
        Q <= l;
      end if;
    end process;
  end behavior;
```

48

Describing a 4-bit Register in Verilog

- Module
 - 4 data inputs, 4 data outputs, and a clock input
 - Define data inputs/outputs as vectors
 - input [3:0] I
 - l<=4'b1000 assigns I[3]=1, I[2]=0, I[1]=0, I[0]=0
 - Output defined as register to store value
- "always" procedure sensitive to positive (rising) edge of clock
 - Sets output Q to input I

```
module Reg4(I, Q, clk);
  input [3:0] I;
  input clk;
  output [3:0] Q;
  reg [3:0] Q;

  always @(posedge clk)
  begin
    Q <= I;
  end
endmodule
```

49

Describing a 4-bit Register in SystemC

- Module
 - 4 data inputs, 4 data outputs, and a clock input
 - Define data inputs/outputs as vectors
 - sc_in<sc_lv<4>> > I;
 - l<="1000" assigns I[3]=1, I[2]=0, I[1]=0, I[0]=0
 - Constructor calls seq_logic method, sensitive to positive (rising) edge of clock
 - seq_logic writes output Q with input I
 - Output port is signal, and signal has storage, thus output retains value

```
#include "systemc.h"
SC_MODULE(Reg4)
{
  sc_in<sc_lv<4>> > I;
  sc_out<sc_lv<4>> > Q;
  sc_in<sc_logic> clk;

  SC_CTOR(Reg4)
  {
    SC_METHOD(seq_logic);
    sensitive_pos << clk;
  }

  void seq_logic()
  {
    Q.write(I.read());
  }
};
```

50

Describing an Oscillator in VHDL

- Entity
 - Defines clock output
- Architecture
 - Process
 - Has no sensitivity list, so executes non-stop as infinite loop
 - Sets clock to 0, waits 10 ns, sets clock to 1, waits 10 ns, repeats

```
library ieee;
use ieee.std_logic_1164.all;

entity Osc is
  port ( clk: out std_logic );
end Osc;

architecture behavior of Osc is
begin
  process
  begin
    clk <= '0';
    wait for 10 ns;
    clk <= '1';
    wait for 10 ns;
  end process;
end behavior;
```

51

Describing an Oscillator in Verilog

- Module
 - Has one output, clk
 - Declare as "reg" to hold value
 - "always" procedure
 - Has no sensitivity list, so executes non-stop as infinite loop
 - Sets clock to 0, waits for 10 ns, sets clock to 1, waits for 10 ns, repeats

```
module Osc(clk);
  output clk;
  reg clk;

  always
  begin
    clk <= 0;
    #10;
    clk <= 1;
    #10;
  end
endmodule
```

52

Describing an Oscillator in SystemC

- Module
 - Has one output, clk
 - Constructor creates single thread
 - Thread consists of infinite loop
 - while (true) {
 - SC_THREAD(seq_logic);
 - }
 - Sets clock to 0, waits 10 ns, sets clock to 1, waits 10 ns, repeats


```
#include "systemc.h"
SC_MODULE(Osc)
{
  sc_out<sc_logic> clk;

  SC_CTOR(Osc)
  {
    SC_THREAD(seq_logic);
  }

  void seq_logic()
  {
    while(true) {
      clk.write(SC_LOGIC_0);
      wait(10, SC_NS);
      clk.write(SC_LOGIC_1);
      wait(10, SC_NS);
    }
  }
};
```

53

Describing a Controller in VHDL

 

- FSM behavior captured using architecture with 2 processes
 - First process models state register
 - Asynchronous reset sets state to "S_Off"
 - Rising clock edge sets currentstate to nextstate
 - Second process models combinational logic
 - Sensitive to currentstate and FSM inputs
 - Sets FSM outputs based on currentstate
 - Sets nextstate based on currentstate and present FSM input values
 - Note declaration of new type, statetype

```
library ieee;
use ieee.std_logic_1164.all;


entity LaserTimer is
  port (b: in std_logic;
        c: in std_logic;
        x: out std_logic;
        y: out std_logic);
end LaserTimer;

architecture behavior of LaserTimer is
  type statetype is
    (S_Off, S_On1, S_On2, S_On3);
  signal currentstate, nextstate:
    statetype;
  begin
    statereg: process(clk, rst)
    begin
      if (rst='1') then -- initial state
        currentstate <= S_Off;
      elsif (clk='1' and clk event) then
        currentstate <= nextstate;
      end if;
    end process;

    comblogic: process (currentstate, b)
    begin
      case currentstate is
        when S_Off =>
          x <= '0'; -- laser off
          if (b='0') then
            nextstate <= S_Off;
          else
            nextstate <= S_On1;
          end if;
        when S_On1 =>
          x <= '1'; -- laser on
          nextstate <= S_On2;
        when S_On2 =>
          x <= '1'; -- laser still on
          nextstate <= S_On3;
        when S_On3 =>
          x <= '1'; -- laser still on
          nextstate <= S_Off;
      end case;
    end process;
  end behavior;
```

54

Describing a Controller in Verilog

 

- FSM behavior captured using 2 "always" procedures
 - First procedure models state register
 - Asynchronous reset sets state to "S_Off"
 - Rising clock edge sets currentstate to nextstate
 - Second process models combinational logic
 - Sensitive to currentstate and FSM inputs
 - Sets FSM outputs based on currentstate
 - Sets nextstate based on currentstate and present FSM input values
- Note state register size must be explicit – 2 bits, reg [1:0] currentstate

```

module LaserTimer(b, x, clk, rst);
  input b, clk, rst;
  output s;
  reg s;


  parameter s_Off = 2'b00,
            s_On1 = 2'b01,
            s_On2 = 2'b10,
            s_On3 = 2'b11;

  reg [1:0] currentstate;
  reg [1:0] nextstate;
  // state register procedure
  always @(posedge rst or posedge clk)
  begin
    if (rst==1) // Initial state
      currentstate <= s_Off;
    else
      currentstate <= nextstate;
  end
  // combinational logic procedure
  always @(currentstate or b)
  begin
    case (currentstate)
      s_Off: begin
        x <= 0; // laser off
        if (b==0)
          nextstate <= s_Off;
        else
          nextstate <= s_On1;
      end
      s_On1: begin
        x <= 1; // laser on
        nextstate <= s_On2;
      end
      s_On2: begin
        x <= 1; // laser still on
        nextstate <= s_On3;
      end
      s_On3: begin
        x <= 1; // laser still on
        nextstate <= s_Off;
      end
    endcase
  end
endmodule

```

55

Describing a Controller in SystemC

 

- FSM behavior captured using 2 methods
 - First method models state register
 - Asynchronous reset sets state to "S_Off"
 - Rising clock edge sets currentstate to nextstate
 - Second process models combinational logic
 - Sensitive to currentstate and FSM inputs
 - Sets FSM outputs based on currentstate
 - Sets nextstate based on currentstate and present FSM input values
- Note use of new type, statetype

```

#include "systemc.h"
enum statetype { s_Off, s_On1, s_On2, s_On3 };
SC_MODULE(LaserTimer)
{
  sc_in<sc_logic> b, clk, rst;
  sc_out<sc_logic> s;
  sc_signal<statetype> currentstate, nextstate;
  SC_CTOR(LaserTimer) {
    SC_METHOD(stateReg);
    SC_METHOD(combLogic);
    sensitive << currentstate << b;
  }
  void stateReg() {
    if (rst.read() == SC_LOGIC_1)
      currentstate = s_Off; // Initial state
    else
      currentstate = nextstate;
  }
  void combLogic() {
    switch (currentstate) {
      case s_Off:
        x.write(SC_LOGIC_0); // laser off
        if (b.read() == SC_LOGIC_0)
          nextstate = s_Off;
        else
          nextstate = s_On1;
        break;
      case s_On1:
        x.write(SC_LOGIC_1); // laser on
        nextstate = s_On2;
        break;
      case s_On2:
        x.write(SC_LOGIC_1); // laser still on
        nextstate = s_On3;
        break;
      case s_On3:
        x.write(SC_LOGIC_1); // laser still on
        nextstate = s_Off;
        break;
    }
  }
};

```

Datapath Component Description using Hardware Description Languages


- Will consider description of three datapath components
 - Full-adders
 - Carry-ripple adders
 - Up-counter

9.4

57

Describing a Full-Adder in VHDL

 - Entity
 - Declares inputs/outputs
- Architecture
 - Described behaviorally (could have been described structurally)
 - Process sensitive to inputs
 - Computes expressions, sets outputs



```

library ieee;
use ieee.std_logic_1164.all;

entity FullAdder is
  port ( a, b, ci: in std_logic;
         s, co: out std_logic );
end FullAdder;

architecture behavior of FullAdder is
begin
  process (a, b, ci)
  begin
    s <= a xor b xor ci;
    co <= (b and ci) or (a and ci) or (a and b);
  end process;
end behavior;

```

58

Describing a Full-Adder in Verilog

- Module
 - Declares inputs/outputs
 - Described behaviorally (could have been described structurally)
 - "always" procedure
 - Sensitive to inputs
 - Computes expressions, sets outputs

```

s = a xor b xor ci
co = bc + ac + ab

module FullAdder(a, b, ci, s, co);
  input a, b, ci;
  output s, co;
  reg s, co;


  always @(a or b or ci)
  begin
    s <= a ^ b ^ ci;
    co <= (b & ci) | (a & ci) | (a & b);
  end
endmodule

```

59

Describing a Full-Adder in SystemC

 - Module
 - Declares inputs/outputs
 - Described behaviorally (could have been described structurally)
 - comblogic method
 - Computes expressions, sets outputs



```


#include "systemc.h"
SC_MODULE(FullAdder)
{
  sc_in<sc_logic> a, b, ci;
  sc_out<sc_logic> s, co;
  SC_CTOR(FullAdder)
  {
    SC_METHOD(combLogic);
    sensitive << a << b << ci;
  }
  void combLogic()
  {
    s.write(a.read() ^ b.read() ^ ci.read());
    co.write((b.read() & ci.read()) |
             (a.read() & ci.read()) |
             (a.read() & b.read()));
  }
};

```

60

Describing a Carry-Ripple Adder in VHDL

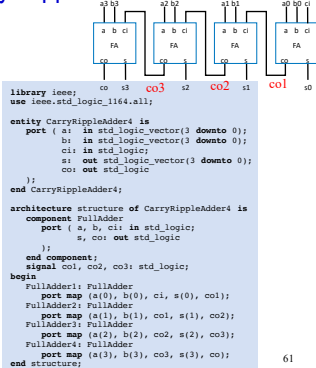
- Entity
 - Declares inputs/outputs
 - Uses `std_logic_vector` for 4-bit inputs/outputs
- Architecture
 - Described structurally by composing four full-adders (could have been described behaviorally instead)
 - Declares full-adder component, instantiates four full-adders, connects
 - Note use of three internal signals for connecting carry-out of one stage to carry-in of next stage



61

Describing a Carry-Ripple Adder in Verilog

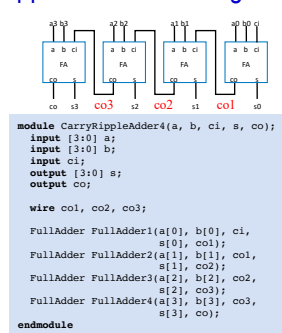
- Module
 - Declares inputs/outputs
 - Uses vectors for 4-bit inputs/outputs
 - Described structurally by composing four full-adders (could have been described behaviorally instead)
 - Instantiates four full-adders, connects
 - Note use of three internal wires for connecting carry-out of one stage to carry-in of next stage



62

Describing a Carry-Ripple Adder in SystemC


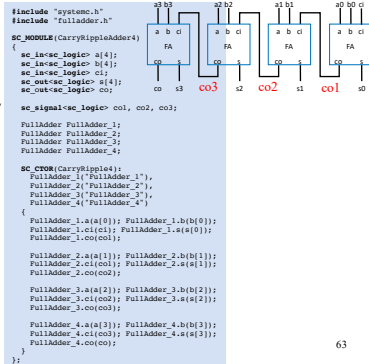
- Module
 - Declares inputs/outputs
 - Uses vectors for 4-bit inputs/outputs
 - Described structurally by composing four full-adders (could have been described behaviorally instead)
 - Instantiates four full-adders, connects
 - Note use of three internal wires for connecting carry-out of one stage to carry-in of next stage



63

Describing an Up-Counter in VHDL

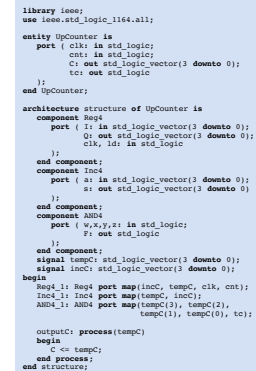
 
- Described structurally (could have been described behaviorally)
- Includes process that updates output port C whenever internal signal tempC changes
 - Need tempC signal because can't read C due to C being an output port



64

Describing an Up-Counter in Verilog

 
 
- Described structurally (could have been described behaviorally)
- Includes always procedure that updates output C whenever internal wire tempC changes
 - Need tempC wire because can't use C in the connection statements



65

Describing an Up-Counter in SystemC

  - Described structurally (could have been described behaviorally)
- Includes method that updates output C whenever internal signal tempC changes
 - Need tempC signal because can't use C in the connection statements
- Can't use logic vector bits individually for connections, so needed tempC_b array too



66

RTL Design using Hardware Description Languages


9.5

- Will consider two forms of RTL descriptions
 - High-level state machine
 - Controller and datapath

67


HLSM of Laser-Based Dist. Measurer: VHDL

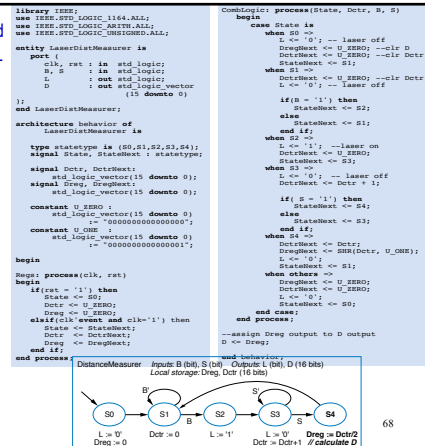- Architecture similar to FSM
 - Curr/next sigs for all regs
- Asynch reset forces to state S0
- Rising clock
 - Perform state's computation
 - Prepare to go to next state based on state and inputs
- Concurrent sig assignment sets D to Dreg always



68

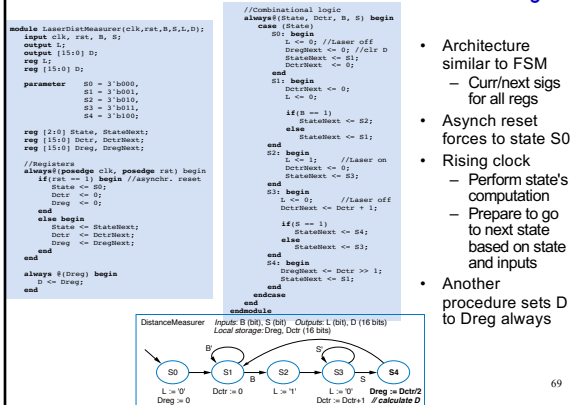
HLSM of Laser-Based Distance Measurer: Verilog



69

HLSM of Laser-Based Distance Measurer: SystemC

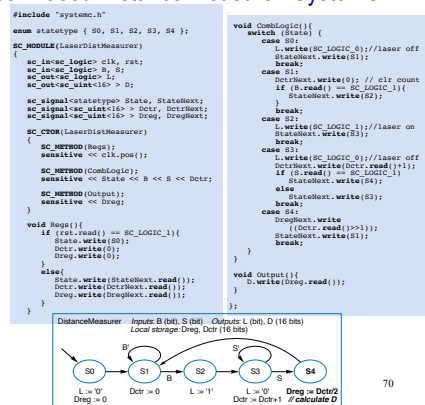
- Architecture similar to FSM
 - Curr/next sigs for all regs
- Asynch reset forces to state S0
- Rising clock
 - Perform state's computation
 - Prepare to go to next state based on state and inputs
- Another process sets D to Dreg always



70


Controller and DP of Laser-Based Distance Measurer in VHDL

 - At highest level, just connection of controller and datapath components




71

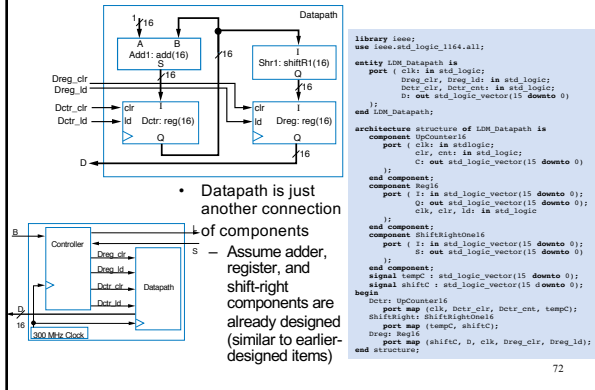DP of Laser-Based Distance Measurer in VHDL



72

 Controller of Laser-Based Distance Measurer: VHDL



- FSM similar to high-level state machine
 - But high-level operations replaced by low-level datapath signals
 - Use two-process FSM description approach

```
library ieee;
use ieee.std_logic_1164.all;

entity LDM_Controller is
    port (
        clk, rst, in_std_logic: in std_logic;
        L: out std_logic;
        Dreg_clr, Dreg_id: out std_logic;
        Dctr_clr, Dctr_id: out std_logic
    );
end LDM_Controller;

architecture behavior of LDM_Controller is
    type state_type is (S0, S1, S2, S3, S4);
    signal currentstate, nextstate: state_type;


    begin
        process (clk, rst)
        if (rst='1') then
            currentstate <= S0; -- initial state
        elsif (clk='1' and clk'event) then
            currentstate <= nextstate;
        end if;
        end process;

        process (currentstate, B, S)
        begin
            case currentstate is
                when S0 =>
                    L <= '0'; -- laser off
                    Dreg_clr <= '1'; -- clr Dreg
                    nextstate <= S1;
                when S1 =>
                    Dctr_clr <= '1'; -- clr count
                    if (B='1') then
                        nextstate <= S2;
                    end if;
                when S2 =>
                    L <= '1'; -- laser on
                    nextstate <= S3;
                when S3 =>
                    L <= '0'; -- laser off
                    Dctr_id <= '1'; -- count up
                    if (S='1') then
                        nextstate <= S4;
                    end if;
                when S4 =>
                    Dreg_id <= '1'; -- load Dreg
                    nextstate <= S0;
            end case;
        end process;
    end behavior;
```

```
combiogic: process(currentstate, B, S)
begin
    L <= '0';
    Dreg_clr <= '1';
    Dreg_id <= '0';
    Dctr_clr <= '0';
    Dctr_id <= '0';
    case currentstate is
        when S0 =>
            L <= '0'; -- laser off
            Dreg_clr <= '1'; -- clr Dreg
            nextstate <= S1;
        when S1 =>
            Dctr_clr <= '1'; -- clr count
            if (B='1') then
                nextstate <= S2;
            end if;
        when S2 =>
            L <= '1'; -- laser on
            nextstate <= S3;
        when S3 =>
            L <= '0'; -- laser off
            Dctr_id <= '1'; -- count up
            if (S='1') then
                nextstate <= S4;
            end if;
        when S4 =>
            Dreg_id <= '1'; -- load Dreg
            nextstate <= S0;
        end case;
    end process;
end behavior;
```

Controller and DP of Laser-Based Distance Measurer: Verilog

 - At highest level, just connection of controller and datapath components




```
module LaserDistMeasurer(clk,rst,B,S,L,D);
    input clk, rst, B, S;
    output L;
    output [15:0] D;
    wire Dreg_clr, Dreg_id;
    wire Dctr_clr, Dctr_id;

    LDM_Controller
        LDM_Controller_1(clk, rst, B, S, L,
            Dreg_clr, Dreg_id,
            Dctr_clr, Dctr_id);

    LDM_Datapath
        LDM_Datapath_1(clk, Dreg_clr, Dreg_id,
            Dctr_clr, Dctr_id, D);
endmodule
```

74

 DP of Laser-Based Distance Measurer: Verilog



- Datapath just another connection of components
 - Assume adder, register, and shift-right components are already designed (similar to earlier-designed items)

```
module Add16(A, B, S);
    input [15:0] A, B;
    output [15:0] S;
    //details not shown
endmodule

module Reg16(I, Q, clk, clr, ld);
    input [15:0] I;
    input clk, clr, ld;
    output [15:0] Q;
    //details not shown
endmodule


module shiftR16(I, S);
    input [15:0] I;
    input [15:0] S;
    output [15:0] Q;
    //details not shown
endmodule

module LDM_Datapath(clk, Dreg_clr, Dreg_id,
    Dctr_clr, Dctr_id, D);
    input clk;
    input Dreg_clr, Dreg_id;
    input Dctr_clr, Dctr_id;
    output [15:0] D;

    wire [15:0] addc, tempc, shiftc;
    Reg16 Dctr_reg(addc, tempc, clk, Dctr_clr, Dctr_id);
    shiftR16 Dctr_shift(tempc, shiftc);
    Reg16 Dreg_reg(shiftc, D, clk, Dreg_clr, Dreg_id);
endmodule
```

75

 Controller of Laser-Based Distance Measurer: Verilog



- FSM similar to high-level state machine
 - But high-level operations replaced by low-level datapath signals
 - Use two-procedure FSM description approach

```
module LDM_Controller
    (clk, rst, B, S, L, Dreg_clr, Dreg_id,
     Dctr_clr, Dctr_id);
    input clk, rst, B, S;
    output L;
    output [15:0] D;
    output Dreg_clr, Dreg_id;
    output Dctr_clr, Dctr_id;
    reg [15:0] D;
    parameter S0 = 3'b000,
              S1 = 3'b001,
              S2 = 3'b010,
              S3 = 3'b011,
              S4 = 3'b100;
    reg [2:0] State;
    reg [2:0] StateNext;


    always @(posedge rst or posedge clk)
    if (rst==1)
        State <= S0; // initial state
    else
        State <= StateNext;
    end

    begin
        State <= StateNext;
    end
endmodule
```

```
always @(State or B or S)
begin
    L <= 0;
    Dreg_clr <= 0;
    Dreg_id <= 0;
    Dctr_clr <= 0;
    Dctr_id <= 0;
    case (State)
        S0: begin
            L <= 0; // laser off
            Dreg_clr <= 1; // clr Dreg
            StateNext <= S1;
        end
        S1: begin
            Dctr_clr <= 1; // clr count
            if (B==1)
                StateNext <= S2;
            else
                StateNext <= S1;
        end
        S2: begin
            L <= 1; // laser on
            StateNext <= S3;
        end
        S3: begin
            L <= 0; // laser off
            Dctr_id <= 1; // count up
            if (S==1)
                StateNext <= S4;
            else
                StateNext <= S3;
        end
        S4: begin
            Dreg_id <= 1; // load Dreg
            Dctr_id <= 0; // stop count
            StateNext <= S0;
        end
    endcase
end
endmodule
```

Controller and DP of Laser-Based Distance Measurer: SystemC

 - At highest level, just connection of controller and datapath components



```
#include "systemc.h"
#include "LDM_Controller.h"
#include "LDM_Datapath.h"

SC_MODULE(LaserDistMeasurer) {
    sc_in<sc_logic> clk, rst;
    sc_in<sc_logic> B, S;
    sc_out<sc_logic> L;
    sc_out<sc_int<16>> D;


    sc_signal<sc_logic> Dreg_clr, Dreg_id;
    sc_signal<sc_logic> Dctr_clr, Dctr_id;

    LDM_Controller LDM_Controller_1;
    LDM_Datapath LDM_Datapath_1;

    SC_Clock(LDM_Controller_1) {
        LDM_Controller_1.clk(clk);
        LDM_Controller_1.rst(rst);
        LDM_Controller_1.B(B);
        LDM_Controller_1.S(S);
        LDM_Controller_1.Dreg_clr(Dreg_clr);
        LDM_Controller_1.Dreg_id(Dreg_id);
        LDM_Controller_1.Dctr_clr(Dctr_clr);
        LDM_Controller_1.Dctr_id(Dctr_id);
        LDM_Datapath_1.clk(clk);
        LDM_Datapath_1.Dreg_clr(Dreg_clr);
        LDM_Datapath_1.Dreg_id(Dreg_id);
        LDM_Datapath_1.Dctr_clr(Dctr_clr);
        LDM_Datapath_1.Dctr_id(Dctr_id);
        LDM_Datapath_1.D(D);
    }
};
```

77

 DP of Laser-Based Distance Measurer: SystemC



- Datapath just another connection of components
 - Assume adder, register, and shift-right components are already designed (similar to earlier-designed items)

```
#include "systemc.h"
#include "Add16.h"
#include "Reg16.h"
#include "shiftR16.h"


SC_MODULE(LDM_Datapath) {
    sc_in<sc_logic> clk;
    sc_in<sc_logic> Dreg_clr, Dreg_id;
    sc_in<sc_logic> Dctr_clr, Dctr_id;
    sc_out<sc_int<16>> D;

    sc_signal<sc_int<16>> tempc;
    sc_signal<sc_int<16>> addc;
    sc_signal<sc_int<16>> shiftc;

    Add16 Add1;
    Reg16 Dctr_reg;
    shiftR16 Dctr_shift;

    SC_Clock(LDM_Datapath) {
        Dctr_reg.clk(clk);
        Dctr_shift.clk(clk);
        Add1.clk(clk);
        Add1.B(tempc);
        Add1.A(addc);
        Dctr_reg.I(shiftc);
        Dctr_reg.D(D);
        Dctr_reg.Dctr_clr(Dctr_clr);
        Dctr_reg.Dctr_id(Dctr_id);
        Dctr_reg.Dctr_id(Dctr_id);
        Dctr_reg.Dctr_id(Dctr_id);
        Dctr_reg.Dctr_id(Dctr_id);
    }
};
```

 Controller of Laser-Based Distance Measurer: SystemC



- FSM similar to high-level state machine
 - But high-level operations replaced by low-level datapath signals
 - Use two-procedure FSM description approach

```

#include "systemc.h"

enum statetype { S0, S1, S2, S3, S4 };
SC_MODULE(LDM_Controller)
{
    sc_in<sc_logic> clk, rst, B, S;
    sc_out<sc_logic> L;
    sc_out<sc_logic> Dreg_clr, Dreg_id;
    sc_out<sc_logic> Dctr_clr, Dctr_id;
    sc_signal<statetype> State, StateNext;
    SC_CTOR(LDM_Controller)
    {
        SC_METHOD(statereg);
        sensitive << clk.pos();
    }
    SC_METHOD(comblogic);
    sensitive << State << B << S;
}

void statereg() {
    if (rst.read()) == SC_LOGIC_1 {
        State = S0; // Initial state
    }
    else {
        State = StateNext;
    }
}

```

```

void comblogic() {
    L.write(SC_LOGIC_0);
    Dreg_clr.write(SC_LOGIC_0);
    Dreg_id.write(SC_LOGIC_0);
    Dctr_clr.write(SC_LOGIC_0);
    Dctr_id.write(SC_LOGIC_0);

    switch (State) {
        case S0:
            L.write(SC_LOGIC_0); // laser off
            Dreg_clr.write(SC_LOGIC_0);
            break;
        case S1:
            Dctr_clr.write(SC_LOGIC_1);
            if (B.read() == SC_LOGIC_1)
                StateNext.write(S1);
            else
                StateNext.write(S2);
            break;
        case S2:
            L.write(SC_LOGIC_1); // laser on
            StateNext.write(S3);
            break;
        case S3:
            L.write(SC_LOGIC_0); // laser off
            Dctr_id.write(SC_LOGIC_1);
            if (S.read() == SC_LOGIC_1)
                StateNext.write(S4);
            else
                StateNext.write(S3);
            break;
        case S4:
            Dreg_id.write(SC_LOGIC_1);
            Dctr_id.write(SC_LOGIC_0);
            StateNext.write(S1);
            break;
    }
}

```

Summary

- Programmable processors are widely used
 - Easy availability, short design time
- Basic architecture
 - Datapath with register file and ALU
 - Control unit with PC, IR, and controller
 - Memories for instructions and data
 - Control unit fetches, decodes, and executes
- Three-instruction processor with machine-level programs
 - Extended to six instructions
 - Real processors have dozens or hundreds of instructions
 - Extended to access external pins
 - Modern processors are far more sophisticated
- Hardware Description Languages (HDLs)
 - VHDL, Verilog, and SystemC are popular
 - Introduced languages mainly through examples

80